

Kammavari Sangham (R) 1952
K. S. GROUP OF INSTITUTIONS

K. S. POLYTECHNIC

Approved by AICTE, New Delhi; Recognized by DTE, Govt., of Karnataka
#15, Near Vajarahalli, Mallasandra, off kanakapura Road, Bengaluru – 560109



Logic Design using Verilog : 20EC32P Lab Manual

Prepared by:

Mr. Chidananda D.ECE., B.E., M.Tech
(Senior Lecturer, Dept. of E&C Engg.)



Government of Karnataka
DEPARTMENT OF COLLEGIATE AND TECHNICAL EDUCATION

Programme	Electronics and Communication	Semester	III
Course Code	20EC32P	Type of Course	Program Core
Course Name	Logic Design using Verilog	Contact Hours	8 hours/week 104 hours/semester
Teaching Scheme	L:T:P :: 3:1:4	Credits	6
CIE Marks	60	SEE Marks	40

1. Rationale

Digital Electronics is a field of electronics involving the study of digital signals and engineering of devices that use or produce them. It is very important in today's life because if digital circuits are used instead of analog circuits the signals can be transmitted without degradation due to noise. Also in a digital system information stored is easier than that of analog systems. The functionality of digital circuits can be changed easily with the help of software without changing the actual circuit. Verilog, a Hardware Description Language, is used for describing digital electronic circuits and systems. It is used for verification of digital circuits through simulation, for timing analysis, for test analysis and for logic synthesis.

2. Course Outcomes: On successful completion of the course, the students will be able to:

CO-01	List the types of Verilog modeling and the use of each model for specific application
CO-02	Design and construct a sequential circuit for a given application and test the circuit to obtain the desired result/output.
CO-03	Compare and contrast combinational and sequential circuits and simulate a given circuit using Verilog descriptions to test to obtain the desired result/output
CO-04	List the various types of A to D, D to A converters along with memory and for a given application select the appropriate converters and/or memory types to be used to obtain the given result/output.

3. Course Content

Week	CO	PO	Lecture (Knowledge Criteria)	Tutorial (Activity Criteria)	Practice (Performance Criteria)
			3 hours/week	1 hour/week	4 hours/week (2 hours/batch twice in a week)
1	1	1,4,5, 6,7	1. VLSI - Introduction, Importance & Need. HDL- Introduction, Importance, Need & Types. 2. Introduction to Verilog HDL, Types of modeling- Switch level, Structural, Data flow and Behavioral. 3. Basic Concepts- Lexical conventions, comments, keywords, identifiers, strings.	Refer Table 1	1. Familiarization of Xilinx software. 2. Familiarization of FPGA/CPLD KIT.

2	1	1,2,4	<p>1. Data types -Value Set, Wires, Nets, Registers, Vectors, Integers, Real, Time, Parameters, Arrays, Strings.</p> <p>2. Operators- Arithmetic, Logical, Relational, Bit-wise.</p> <p>3. Reduction, Shift, Concatenation, Replication, Conditional operators. Operator Precedence.</p>	Refer Table 1	<p>1. Demonstrate and Practice simple examples using different data types.</p> <p>2. Compute the output for expressions having different operators using simple programs.</p>
3	1,3	1,2,3,6	<p>1. Program structure- Module declaration, port declaration, port connection.</p> <p>2. Gate level modeling for basic gates.</p> <p>3. Gate level Verilog description for half adder, full adder.</p>	Refer Table 1	<p>Write the verilog code, simulate and download to FPGA/CPLD kit for the following</p> <p>1. 2 input basic gates using gate level modelling.</p> <p>2. Full adder and full subtractor using gate level modelling.</p>
4	1,3	1,2,3,4,6	<p>1. Data flow modeling- Continuous assignment, Module instantiations, net declaration, delays, expressions.</p> <p>2. Data flow Verilog description of multiplexer and demultiplexer.</p> <p>3. Data flow Verilog description for 4-bit comparator</p>	Refer Table 1	<p>Write the verilog code, simulate and download to FPGA/CPLD kit for the following.</p> <p>1. 4:1 Mux and 1:4 Demux using data flow modeling.</p> <p>2. Comparator using data flow modeling.</p>
5	1,3	2,3,4,6	<p>1. System tasks-display, strobe, monitor, reset, stop, finish. Compiler directives- include, define. Behavioral modeling- Always and Initial statements.</p> <p>2. Procedural Assignments- Blocking and non-blocking assignments. Timing Control-Delay, Event</p> <p>3. Conditional statements-if, if-else, Case, Loops- While, For, Repeat, Forever.</p>	Refer Table 1	<p>1a. Write and execute simple programs to illustrate conditional statements.</p> <p>1b. Write and execute simple programs to illustrate loops.</p> <p>2. Write the verilog code, simulate and download to FPGA/CPLD kit for a 4-bit ALU with any 2 arithmetic and logical operations.</p>
6	1,3	1,2,3,4,6	<p>1. Behavioral Verilog description for BCD to seven segment decoder for common anode display using if-else, Case.</p> <p>2. Traffic light controller using Behavioral description.</p> <p>3. Test bench- Need, Importance, testbench for half adder.</p>	Refer Table 1	<p>1. Write the verilog code, simulate and download to FPGA/CPLD kit for a BCD to seven segment decoder using case statement.</p> <p>2. Write and simulate a Test bench for half adder.</p>

7	2	1,2,3,4,6,7	<p>1. Sequential circuits - Introduction. Flip flops- types, SR flip flop- Gate level circuit using NAND gates, truth table, working, timing diagram.</p> <p>2. JK, JK-MS flip flops-Logic circuit, truth table, working, timing diagram.</p> <p>3. D, T flip flops-Logic circuit, truth table, working, timing diagram. Relevance of Asynchronous inputs to flip-flops.</p>	Refer Table 1	<p>1. Construct and test clocked SR Flip flop using NAND gates in digital trainer kit.</p> <p>2. Implement D and T Flip flops using JK flip flop in digital trainer kit and observe the timing diagram.</p>
8	2,3	1,2,3,4	<p>1. Verilog description of SR flip flops using data flow modeling.</p> <p>2. Verilog description of JK flip flop using behavioral modeling.</p> <p>3. Registers- Classification of registers, realization of simple (3 or 4 bit) SISO using flip-flops.</p>	Refer Table 1	<p>Write the verilog code, simulate and download to FPGA/CPLD kit for the following.</p> <p>1. SR, JK flip flops using data flow modeling 2.D, T flip flops using behavioral modeling</p>
9	2,3	1,2,3,4,6,7	<p>1. Realization of SIPO, PISO and PIPO using flip flops.</p> <p>2. Concept of universal shift-register. Ring counter and Johnson's counter (3 bit).</p> <p>3. Verilog description of any one shift register using any modeling.</p>	Refer Table 1	<p>Construct and verify the working of the following using suitable IC in digital trainer kit</p> <p>1. SISO, SIPO, PISO and PIPO(4-bit) shift registers. 2. Ring and Johnson counter(4-bit).</p>
10	3	1,3,4,6,7	<p>1. Counters - definition, classification, modulus. Working and realization of asynchronous (3 bit/4 bit) counters using flip-flops.</p> <p>2. Working and realization of synchronous (3-bit/ 4-bit) counters and their comparison.</p> <p>3. Realization of partial mod (mod n) counters-asynchronous, synchronous.</p>	Refer Table 1	<p>Construct and verify the working of the following using digital trainer kit</p> <p>1. 3 bit ripple counter using IC 7476. 2. 4 bit counter as a frequency divider.</p>
11	3,4	1,2,6,7	<p>1. Realization of higher-mod counters using lower-mod counters. Concept of up/ down counters.</p> <p>2. Verilog description of any one counter using any modeling.</p> <p>3. Data converters- Need for DAC and ADC, DAC specifications, types, working of Weighted resistor type.</p>	Refer Table 1	<p>1. Write the verilog code, simulate and download to FPGA/CPLD kit for an up/down counter using behavioral modeling.</p> <p>2. Construct/Simulate and verify the working of R-2R DAC.</p>
12	4	1,2,3,4,6,7	<p>1. ADC specifications. types, working of Flash ADC.</p>	Refer Table 1	<p>1. Construct/Simulate and verify the working of Flash ADC.</p>

			2. Working of Successive approximation and dual slope ADCs. 3. Memory devices- Introduction, classification based on different criteria, read and write operations.		2. Illustrate the storing and retrieving of data in RAM using suitable IC.
13	4	1,2,3,4,7	1. Introduction to PLDs- PAL, PLA, CPLD, FPGA, ASIC. IC Design Verification – Types & Stages. 2. PAL- Architecture, Implementation of a Boolean expressions using PAL. 3. PLA-Architecture, Implementation of a Boolean expressions using PLA.	Refer Table 1	1. Implementation of Boolean expressions using PAL. 2. Implementation of Boolean expressions using PLA.
Total in hours			39	13	52

Note: 1) In Practice sessions Video demonstration should be followed by MCQs/Quiz/Subjective questions and the evaluation has to be documented.

2) In Practice sessions, all circuits should be simulated using suitable software before its construction and verification.

TABLE 1: Suggested activities for tutorials

The list is shared as an example and not inclusive of all possible activities of the course.

The list of activities for one week can be shared among teams in a batch of students.

Week No.	Suggested activities for tutorials
01	1. Explain the typical design flow for VLSI IC Circuits. 2. Give a presentation on comparison of different types of HDLs. 3. Give a presentation on comparison of different types of modeling in Verilog.
02	1. Prepare a report on declaration and initialization of variables of different data types in Verilog. 2. Prepare a report on hierarchy of operators.
03	1. Explain basic components of a module? Which components are mandatory? 2. Prepare a report on Hierarchical names for variables. 3. Write and explain a Verilog code for 4:1 mux and 1:4 demux using gate level modeling.

04	<ol style="list-style-type: none"> 1. Write and explain the Verilog code for full adder using data flow modeling. 2 Write and explain the Verilog code for 8:1 mux using data flow modeling.
05	<ol style="list-style-type: none"> 1. Give a presentation on the differences between tasks and functions 2. Illustrate the use of system tasks with examples. 3. Illustrate the use of gate delays to model timing for a simple logic equation.
06	<ol style="list-style-type: none"> 1. Compare if-else and case statements with the help of examples. 2. Compare all loops with the help of examples. 3. Write and explain the verilog code for full subtractor and 1:8 demux using behavioral modeling. 4. Explain the Verilog Test bench with an example to verify the HDL designs.
07	<ol style="list-style-type: none"> 1. Prepare a report on differences between Combinational and Sequential circuits with examples. 2. Give a presentation on application of flip flop as bounce elimination switch. 3. Demonstrate the working of flip flop as a one bit memory element.
08	<ol style="list-style-type: none"> 1. Prepare a report on flip flop ICs and their features. 2. Give a presentation on eliminating race -around condition in JK flip flop. 3. Compare the advantages and disadvantages of all flip flops.
09	<ol style="list-style-type: none"> 1. Prepare a report on shift register ICs and their features. 2. Give a presentation on applications of shift registers in real life. 3. Demonstrate the working of IC 7495 as shift register.
10	<ol style="list-style-type: none"> 1. Prepare a report on differences between asynchronous and synchronous counters. 2. Give a presentation on how counters can be used in a simple car parking system. 3. Give a presentation on implementation of footfall counter for various purposes
11	<ol style="list-style-type: none"> 1. Prepare a report & explain the specifications of DAC and ADC ICs. 2. Give a presentation on any application of DAC in real life. 3. Give a presentation on any application of ADC in real life.

12	<ol style="list-style-type: none"> 1. Prepare a report & explain the types of RAM and ROM. 2. Give a presentation on usage of RAM and ROM in different digital devices.
13	<ol style="list-style-type: none"> 1. Study the latest technological changes in this course and present the impact of these changes on industry. 2. Prepare a report on CPLD, FPGA and ASIC and its applications. 3. Give a presentation on importance or scope of Design Verification in Integrated circuit designs.

LINKS.

1. <https://verilogguide.readthedocs.io/en/latest/verilog/testbench.html>
2. <https://youtu.be/XES0QUi8ttY>(week 11, exp 2)
3. <https://www.youtube.com/watch?v=krmXg-WTbIU> (week 12, exp 1)
4. <http://www.asicguru.com/verilog/tutorial/system-tasks-and-functions/68/>.
5. https://youtu.be/vHlg_QLGIQ (week 7,exp 3)
6. <https://youtu.be/AtX5x53FcLI> (week 9,exp 3)
7. https://youtu.be/Bx_4rsUAGoM
8. <https://www.irisys.net/people-counting>.

4. CIE and SEE Assessment Methodologies

Sl. No	Assessment	Test Week	Duration In minutes	Max marks	Conversion
1.	CIE-1 Written Test	5	80	30	Average of three tests 30
2.	CIE-2 Written Test	9	80	30	
3	CIE-3 Written Test	13	80	30	
4.	CIE-4 Skill Test-Practice	6	180	100	Average of two skill tests 20
5	CIE-5 Skill Test-Practice	12	180	100	
6	CIE-6 Portfolio continuous evaluation of Activity through Rubrics	1-13		10	10
Total CIE Marks					60
Semester End Examination (Practice)			180	100	40
Total Marks					100

5. Format for CIE (1,2,3) Written Test

Course Name	Logic Design Using Verilog	Test	I/II/III	Sem	III/IV
Course Code	20EC32P	Duration	80 Min	Marks	30
Note: Answer any one full question from each section. Each full question carries 10 marks.					
Section	Assessment Questions	Cognitive Levels	Course Outcome	Marks	
I	1				

	2			
II	3			
	4			
III	5			
	6			

Note for the Course coordinator: Each question may have one, two or three subdivisions. Optional questions in each section carry the same weightage of marks, Cognitive level and course outcomes.

5. (a) Format for CIE-4 Skill Test -Practice.

SL. No.	COs	Particulars/Dimension	Marks
1	1	List the types of Verilog modelling and the use of each model for specific application.	20
2	3	Write two Verilog programs on combinational circuits for a given application -40 Marks Simulation - 20 Marks Download to FPGA kit - 10 Marks	70
3	1,3	PortFolio evaluation of Practice sessions through rubrics	10
Total Marks			100

5. (b) Format for CIE-5 Skill Test - Practice.

SL. No.	COs	Particulars/Dimension	Marks
1	2	Write a Sequential circuit for a given application -20 Marks Conduction using DTK -20 Marks Output -10 Marks	50
2	3	Write a Verilog program on Sequential circuits for a given application - 10 Marks Simulation -5 Marks Output - 5 Marks	20
3	4	Identify various types of A to D, D to A converters/ memory for a given application & select the appropriate converters/ memory types needed to obtain the required output.	20
4	2,3,4	Portfolio evaluation of Practice sessions through rubrics.	10
Total Marks			100

6. Rubrics for Assessment of Activity (Qualitative Assessment)

Sl. No.	Dimension	Beginner	Intermediate	Good	Advanced	Expert	Students Score
		2	4	6	8	10	
1		Descriptor	Descriptor	Descriptor	Descriptor	Descriptor	8
2		Descriptor	Descriptor	Descriptor	Descriptor	Descriptor	6
3		Descriptor	Descriptor	Descriptor	Descriptor	Descriptor	2
4		Descriptor	Descriptor	Descriptor	Descriptor	Descriptor	2
Average Marks= (8+6+2+2)/4=4.5							5

Note: Dimension and Descriptor shall be defined by the respective course coordinator as per the activities

7. Reference:

Sl. No.	Description
1	Fundamentals of Digital Logic with Verilog Design by Stephen Brown and Zvonko Vranesic
2	Verilog HDL by Samir Palnikar
3	Introduction to Verilog-Peter M Nyasulu
4	Verilog Tutorial-Deepak Kumar Tala

8. SEE Scheme of Evaluation

SL. No.	COs	Particulars/Dimension	Marks
1	1	List the types of Verilog modelling and the use of each model for specific application	10
2	3	Write a Sequential circuit for a given application -10 Marks Conduction using DTK -10 Marks Output -10 Marks	30
3	2	Write a Verilog program for a given application - 10 Marks Simulation - 10 Marks Download to FPGA kit- - 10 Marks	30
4	4	Identify various types of A to D, D to A converters and memory and for a given application & select the appropriate converters and/or memory types needed to obtain the given output.	10
5	1,2, 3,4	Viva-Voce	20
Total Marks			100

9. Equipment/software list with Specification for a batch of 20 students

Sl. No.	Particulars	Specification	Quantity
1	Computers	Intel Core i5 11th gen/8GB RAM/1 TB HDD/256GB SSD/ Graphics 2 GB	20
2	Xilinx software		
3	Digital trainer kits		20
4	Verilog kits		20
5	Dual trace oscilloscope	20-30MHz	10
6	Digital multimeters		05
7	Patch cards	different length	250
8	Digital IC Tester		02
9	ICs 7400,7402,7404,7408,7432,7486,7442, 7445,7446,7474,7476,7427,7489,7490, 7494,7495,74141,74148,74153,74157, 74155,74193,74194,DAC0808,ADC- 0800,741		10 each

Week-1 Experiment - 1

Aim: Familiarization of Xilinx software

The Xilinx ISE development environment allows an engineer to enter a design in a several source formats, including Verilog. ISE allows the design to be expressed in a hierarchal way as the project develops. This allows the engineer to easily change modules as needed and facilitates easy testing.

In an ISE design, all design files are called SOURCES. A source is a file that specifies part of the overall design. These include HDL files in various formats (Verilog, VHDL, ABLE), schematic entry files, and state diagrams. Other types of sources are things like test fixtures and constraint files. Some source types may be new to you, but they are integral to the ISE approach.

All source files are organized into a hierarchy that starts with the TOP-LEVEL MODULE. There are several ways to enter a working design into ISE. This tutorial will illustrate the preferred method. In the preferred method, the top-level module is a schematic file (.sch). Having a schematic as the top-level module allows all sub modules to be combined in the top-level module as they would be in a block diagram. A top-level schematic module also allows signal markers to be attached to the design more easily. Synthesizing a design in ISE comes down to two things. Gathering all the needed sources, and running processes on those sources. In ISE, a process is an operation that is performed on or with a source file. Different Processes are available for different sources. Selecting a source will enable a list of processes available to that source. Any processes run will be run down the hierarchy.

Design Entry

- Click on Xilinx ISE 9.1 icon.
- Go to file, click on new project and give the project name.
- Select the top level source type as HDL then click on next.
- Select the family name as Spartan2, device name as XC2S30, package name as TQ144 and speed as -6. Then click on next.
- Click on new source then select Verilog module and give the file name and click on next.
- Declare the file name and click on next and finish.
- Now type the given Verilog code on the program window and click on save.
- Double click on Synthesis option to verify any syntax errors in the program.
- Click on view RTL schematic to view the logic diagram for the entered program.
- Ensure that you get a green tick (✓) mark that indicates that there are no errors in the code you entered.
- Right click on module name and select new source, now select test bench waveform to verify the truth table output of the code you entered.
- Give the waveform name, then click on next and finish.
- In the initial timing and clock wizard window select he following options - Rising edge, Combinational clock or internal clock, Then click on next.
- Now a new signal window appears in which we need to manually allocate the data as per the truth table inputs.
- After allocating the data click on save.
- In the source window click on Behavioural simulation and then click processes option and select Xilinx ISE simulator, double click on simulate behavioural model.
- A new window appears with the specified input and corresponding output.
- The obtained output can be verified by comparing the truth table.

Result: Study on Familiarization of Xilinx software is completed successfully

Week-1 Experiment – 2

Aim: Familiarization of FPGA/CPLD Kit

Field Programmable Gate Arrays (FPGAs) are semiconductor devices that are based around a matrix of configurable logic blocks (CLBs) connected via programmable interconnects. FPGAs can be reprogrammed to desired application or functionality requirements after manufacturing. This feature distinguishes FPGAs from Application Specific Integrated Circuits (ASICs), which are custom manufactured for specific design tasks. Although one-time programmable (OTP) FPGAs are available, the dominant types are SRAM based which can be reprogrammed as the design evolves.

The Spartan-II family of FPGAs have a regular, flexible, programmable architecture of Configurable Logic Blocks (CLBs), surrounded by a perimeter of programmable Input/Output Blocks (IOBs). There are four Delay-Locked Loops (DLLs), one at each corner of the die. Two columns of block RAM lie on opposite sides of the die, between the CLBs and the IOB columns. These functional elements are interconnected by a powerful hierarchy of versatile routing Channels. Spartan-II FPGAs are customized by loading configuration data into internal static memory cells. Unlimited reprogramming cycles are possible with this approach. Stored values in these cells determine logic functions and interconnections implemented in the FPGA. Configuration data can be read from an external serial PROM (master serial mode), or written into the FPGA in slave serial, slave parallel, or Boundary Scan modes. Spartan-II FPGAs are typically used in high-volume applications where the versatility of a fast programmable solution adds benefits. Spartan-II FPGAs are ideal for shortening product development cycles while offering a cost-effective solution for high volume production.

Spartan-II FPGAs achieve high-performance, low-cost operation through advanced architecture and semiconductor technology. Spartan-II devices provide system clock rates up to 200 MHz. In addition to the conventional benefits of high volume programmable logic solutions, Spartan-II FPGAs also offer on-chip synchronous single port and dual-port RAM (block and distributed form), DLL clock drivers, programmable set and reset on all flip-flops, fast carry logic, and many other features.

Assigning FPGA Package Pins to IO Markers:

- With the top-level schematic selected in the Sources/Module View tab, expand User Constraints item in the Process View tab, then double-click on Assign Package Pins and click Yes in the following pop-up window.
- UCF file will be opened within Xilinx PACE - a separate program for assigning constraints. Now enter the Location of the I/O pins. The Locations or pin numbers are marked on the Spartan 2 kit, Insert the respective values in the Loc column for the pins to be assigned.
- Save the .ucf file and close the Xilinx PACE window.
- Start by expand the Generate Programming File item in the processes view and double-click on Configure Device (iMPACT).
- On the Configure Devices dialog box that appears, ensure Boundary Scan Mode is selected
- Click Next, select Automatically connect to cable and identify Boundary Scan chain and then click Finish
- A new application window (iMPACT) will appear.
- Right click on the xc2s30 IC to assign the configuration file and select the bit file (test.bit) and click open.
- Select the program option and click on Ok.

Result: Study on Familiarization of FPGA/CPLD Kit is completed successfully

Week-2
Experiment - 1

Aim: Demonstrate and Practice simple examples using different data types

Verilog Description for two input Arithmetic operations

Consider the below Arithmetic operations

$$Y1 = A+B$$

$$Y2 = A-B$$

$$Y3 = A*B$$

$$Y4 = A/B$$

$$Y5 = A\%B$$

Verilog Code:

```
module Arithmetic (A, B, Y1, Y2, Y3, Y4, Y5);
  input [2:0] A, B;
  output [4:0] Y1, Y2, Y3, Y4, Y5;
  reg [4:0] Y1, Y2, Y3, Y4, Y5;
  always @(A or B)
  begin
    Y1=A+B; //addition
    Y2=A-B; //subtraction
    Y3=A*B; //multiplication
    Y4=A/B; //division
    Y5=A%B; //modulus of A divided by B
  end
endmodule.
```


Result : Practicing simple examples using different data types is completed successfully

Week-2
Experiment - 1


Aim: Compute the output for expressions having different operators using simple programs

Two level combinational circuit

```
module two_level(a, b, c, d, f);
  input a, b, c, d;
  output f;
  wire t1, t2; // intermediate lines
  assign t1 = a & b;
  assign t2 = ~(c | d);
  assign f = ~(t1 & t2);
endmodule
```

 

```
module using_wand(a, b, c, d, f);  
  input a, b, c, d;  
  output f;  
  wand f; // net f declared as wand  
  assign f = a & b;  
  assign f = c | d;  
endmodule
```

 

$$f = t1 \& t2$$


Here, function realized will be
 $f = (A \& B) \& (C | D)$

Week-3

Experiment – 1

Aim : Write the verilog code,simulate and download to FPGA/CPLD kit for the 2 input basic gates using gate level modelling.

Logic Diagram

 

VERILOG Program

AND Gate

```
module andstr(x,y,z);  
input x,y;  
output z;  
and g1(z,x,y);  
endmodule
```

NAND Gate

```
module nandstr(x,y,z);  
input x,y;  
output z;  
nand g1(z,x,y);  
endmodule
```

OR Gate

```
module orstr(x,y,z);  
input x,y;  
output z;  
or g1(z,x,y);  
endmodule
```

NOR Gate

```
modulenorstr(x,y,z);  
input x,y;  
output z;  
nor g1(z,x,y);  
endmodule
```

XOR Gate

```
module xorstr(x,y,z);  
input x,y;  
output z;  
xor g1(z,x,y);  
endmodule
```

XNOR Gate

```
module xnorstr(x,y,z);  
input x,y;  
output z;  
xnor g1(z,x,y);  
endmodule
```

NOT Gate

```
module notstr(x,z);  
input x;  
output z;  
not g1(z,x);  
endmodule
```


Result: output for 2 input basic gates using gate level modeling is verified successfully

Week-3


Experiment - 2

Aim: Write the verilog code, simulate and download to FPGA/CPLD kit for Full adder and full subtractor using gate level modelling.

Logic Diagram

 

Half adder

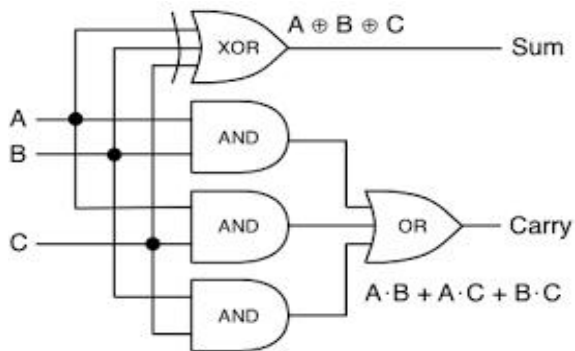

Full adder

Truth table

Half adder

Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full adder

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

VERILOG Program

HALF ADDER:

```
module halfaddstr(sum,carry,a,b);
output sum,carry;
input a,b;
xor(sum,a,b);
and(carry,a,b);
endmodule
```

FULL ADDER:

```
module
fulladdstr(sum,carry,a,b,c);

output sum,carry;

input a,b,c;

xor g1(sum,a,b,c);

and g2(x,a,b);

and g3(y,b,c);


and g4(z,c,a);

or g5(carry,x,z,y);


endmodule
```

Gate level Verilog description for half Subtractor, full Subtractor

Logic Diagram

 

Half subtractor

 

Full Subtractor

Truth Table

Half subtractor

Inputs		Outputs	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Full Subtractor

Inputs			Outputs	
A	B	Borrow _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Verilog Code

HALF SUBTRACTOR:

```
module halfsubtr(diff,borrow,a, b);  
  
output diff,borrow;  
  
input a,b;  
  
xor(diff,a,b);  
  
and( borrow,~a,b);  
  
endmodule
```

FULL SUBTRACTOR:

```
module  
fullsubtr(diff,borrow,a,b,c);  
  
output diff,borrow;  
  
input a,b,c;  
  
wire a0,q,r,s,t;  
  
not(a0,a);  
  
xor(x,a,b);  
  
xor(diff,x,c);  
  
and(y,a0,b);  
  
and(z,~x,c);  
  
or(borrow,y,z);  
  
endmodule
```

Result: output for Full adder and full subtractor using gate level modelling. is verified successfully


Week-4

Experiment – 1

Aim: Write the verilog code, simulate and download to FPGA/CPLD kit for 4:1 Mux and 1:4 Demux using data flow modeling.

4:1 Multiplexer

Logic Diagram

 

Truth Table

Selection Inputs		Outputs			
S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


Verilog Code

```

module MUX41(i0,i1,i2,i3,s0,s1,y);
input i0,i1,i2,i3,s0,s1;
output y;
assign y = ((i0 & ~(s0)) & ~(s1)) | (i1 & ~(s0) & s1) | (i2 & s0 & ~(s1)) | (i3 & s0 & s1);
endmodule

```

1:4 De-Multiplexer

 

Truth Table

Input	Select Lines	Output Lines
I	S ₁ S ₀	D ₀ D ₁ D ₂ D ₃
I	0 0	1 0 0 0
I	0 1	0 1 0 0
I	1 0	0 0 1 0
I	1 1	0 0 0 1

Verilog Code

```
module demux14df(in,d0,d1,d2,d3,s0,s1);  
output d0,d1,d2,d3;  
input in,s0,s1;  
assign d0 = in & (~s0) & (~s1);  
assign d1 = in & (~s0) & s1;  
assign d2 = in & s0 & (~s1);  
assign d3 = in & s0 & s1;  
endmodule
```


Result: output for 4:1 Mux and 1:4 Demux using data flow modeling is verified successfully

Week-4

Experiment – 2

Aim: Write the verilog code, simulate and download to FPGA/CPLD kit for Comparator using data flow modeling.

Block Diagram

 

Truth Table

A3	A2	A1	A0	B3	B2	B1	B0	A>B	A<B	A=B
0	0	0	0	0	0	0	1	0	1	0
0	1	0	1	0	0	1	1	1	0	0
1	0	1	0	1	0	1	0	0	0	1
0	0	1	1	0	1	1	0	0	1	0
0	1	0	0	1	0	0	0	0	1	0
1	1	0	1	1	0	1	1	1	0	0
0	1	1	0	0	1	1	0	0	0	1
1	1	1	1	1	1	1	0	1	0	0

Verilog Code

```
module magcomp (A,B,ALTB,AGTB,AEQB);  
  input [3:0] A,B;  
  output ALTB,AGTB,AEQB;  
  assign ALTB = (A < B), AGTB = (A > B), AEQB = (A == B);  
endmodule
```

Result: output for Comparator using data flow modeling is verified successful


Week-5

Experiment – 1a

Aim: Write and execute simple programs to illustrate conditional statements

Consider 2:1 Mux to illustrate conditional statements

Block Diagram:

 

Truth Table:

Select	Output
S	Y
0	D ₀
1	D ₁

Verilog Code :

```
module mux2to1( D0, D1, sel, Y_out);
    input D0;
    input D1;
    input sel;
    output Y_out;
    reg Y_out;

    always @(D0,D1,sel)
    begin
        if(sel == 0)
            Y_out = D0;
        else
            Y_out = D1;
        end
    endmodule
```

Result: output for program to illustrate conditional statements is verified successfully


Week-5

Experiment – 1b

Aim: Write and execute simple program to illustrate loops.

Consider a 4-bit parallel adder to illustrate verilog code using 'for' loop.

Block Diagram:

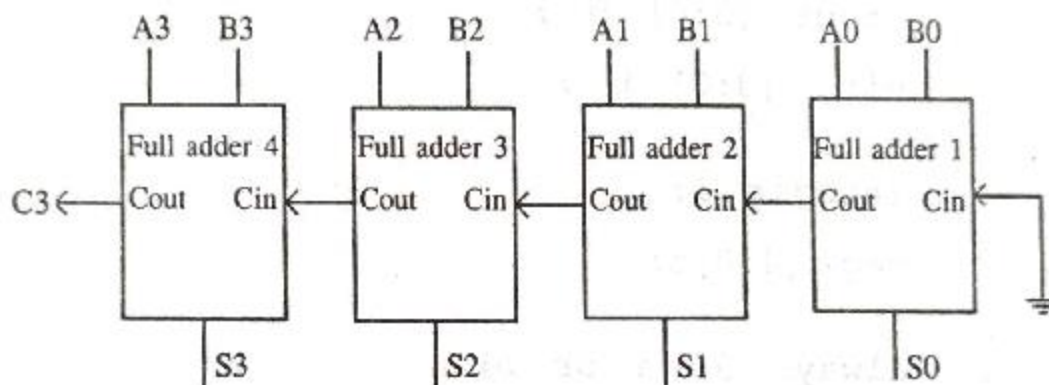

Sample Truth Table:

A3 A2 A1 A0	B3 B2 B1 B0	S3 S2 S1 S0	Cout
1 1 1 0	0 1 1 0	0 1 0 0	1
0 1 0 1	1 0 1 0	1 1 1 1	0

Expressions:

$$S0 = a0 \text{ XOR } b0 \text{ XOR } cin$$

$$c0 = (a0.b0) + (b0.cin) + (a0.cin)$$

Verilog Code:

```
module adder_4bit (a ,b ,sum ,carry);
    output [3:0] sum ;
    reg [3:0] sum ;
```

```

output carry ;
reg carry ;

input [3:0] a ;
wire [3:0] a ;
input [3:0] b ;
wire [3:0] b ;

integer i;
reg [4:0]s;

always @ (a or b)
begin
    s[0] = 0;
    for (i=0;i<=3;i=i+1) begin
        sum [i] = a[i] ^ b[i] ^ s[i];
        s[i+1] = (a[i] & b[i]) | (b[i] &
s[i]) | (s[i] & a[i]);
    end
    carry = s[4];
end
endmodule

```


Result: output for simple program to illustrate loops is verified successfully

Week-5

Experiment – 2

Aim: Write the verilog code, simulate and download to FPGA/CPLD kit for a ALU with any 2 arithmetic and logical operations.

Block Diagram

 

Verilog Code:

```
module alua (a,b,s,y);
input[1:0]a,b,s;
output[1:0]y;
reg[1:0]y;
always @(*)
begin
case (s)
2'b00:y=a+b;
2'b01:y=a-b;
2'b10:y=a&b;
2'b11:y=a|b;
endcase
end
endmodule
```


Result: output for 4-bit ALU with any 2 arithmetic and logical operations is verified successfully

Week-6

Experiment – 1


Aim: Write the verilog code, simulate and download to FPGA/CPLD kit for a BCD to seven segment decoder using case statement.

Block Diagram

 

Truth Table

Decimal Digit	Input lines				Output lines							Display pattern	Individual Segments							Display
	A	B	C	D	a	b	c	d	e	f	g		a	b	c	d	e	f	g	
0	0	0	0	0	1	1	1	1	1	1	0	0	x	x	x	x	x	x	x	0
1	0	0	0	1	0	1	1	0	0	0	0	0	x	x	x	x				1
2	0	0	1	0	1	1	0	1	1	0	1	0	x	x						2
3	0	0	1	1	1	1	1	1	0	0	1	0	x	x						3
4	0	1	0	0	0	1	1	0	0	1	1	1	x	x						4
5	0	1	0	1	1	0	1	1	0	1	1	1	x	x	x	x				5
6	0	1	1	0	1	0	1	1	1	1	1	1	x	x						6
7	0	1	1	1	1	1	1	0	0	0	0	0	x							7
8	1	0	0	0	1	1	1	1	1	1	1	1	x							8
9	1	0	0	1	1	1	1	1	0	1	1	1	x	x	x					9

 

Verilog Code :

```

module case(x,y);
input[3:0]x;
output[6:0]y;
reg[6:0]y;
always @ (x)
begin
case (x)
0 : y =
7'b0000001;
1 : y =
7'b1001111;
2 : y =
7'b0010010;
3 : y =

```

```
7'b0000110;  
    4 : y =  
7'b1001100;  
    5 : y =  
7'b0100100;  
    6 : y =  
7'b0100000;  
    7 : y =  
7'b0001111;  
    8 : y =  
7'b0000000;  
    9 : y =  
7'b0000100;  
default : y = 7'b1111111;  
endcase  
end  
endmodule
```

Result: output for BCD to seven segment decoder using case statement is verified successfully.

Week-6

Experiment – 2

Aim: Write and simulate a Test bench for half adder.

Verilog Code

```
module ha(sum,carry,a,b);
output sum,carry;
input a,b;
xor(sum,a,b);
and(carry,a,b);
endmodule
```

Test Bench

```
module ha_test;
    // Inputs
    reg a;
    reg b;
    // Outputs
    wire sum;
    wire carry;
    // Instantiate the Unit Under Test (UUT)
    ha uut (
        .sum(sum),
        .carry(carry),
        .a(a),
        .b(b)
    );

    initial begin
        // Initialize Inputs
        a = 0;
        b = 0;

        // Wait 100 ns for global reset to finish
        #100;

        a = 0;
        b = 1;

        // Wait 100 ns for global reset to finish
        #100;

        a = 1;
        b = 0;

        // Wait 100 ns for global reset to finish
        #100;


        a = 1;
        b = 1;
    end
endmodule
```

```
// Wait 100 ns for global reset to finish
#100;
// Add stimulus here
```

```
end
```

```
endmodule
```

Simulation

 

Result: Test bench for half adder is simulated successfully.

Week-7 Experiment – 1


Aim :

To Realize and verify the function of clocked SR Flip-Flop using NAND logic gates.


Apparatus Required :

- ☞ Digital trainer kit
- ☞ NAND gate IC 7400
- ☞ Patch chords.

Pin Diagram of IC 7400 NAND Gate

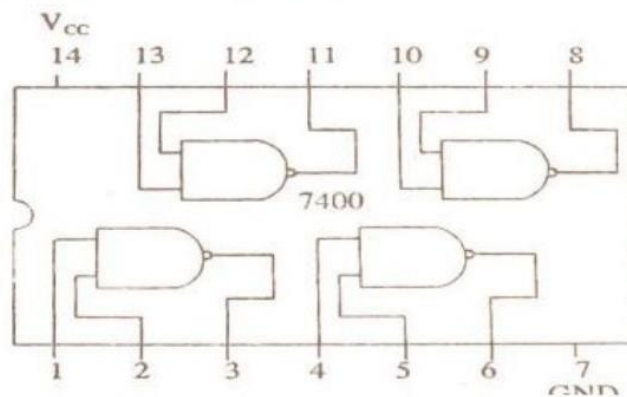

 Circuit Diagram of SR Flip Flop using only NAND gates



Note : Pin 16 = V_{CC} and 7 = GND for IC 7400

Truth Table :

Clock	Q_n Initial State	S	R	Q_{n+1} Next state
0	X	X	X	No Change
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	Indeterminate
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	Indeterminate

Procedure :

1. Check the working of all the components.
2. Insert the appropriate IC into the IC base.
3. Make connections as shown in the circuit diagram.
4. Apply the clock pulse manually, verify the Truth Table and observe the outputs.

Result :

Clocked SR FF is constructed using NAND gates and verified its functionality.

Week-7 Experiment – 2


Aim :

To Realize and verify the truth table of T and D Flip-Flop using JK flip flop IC 7476.


Apparatus Required :

- ☞ Digital trainer kit
- ☞ Flip Flop IC 7476
- ☞ NOT gate IC 7404
- ☞ Patch chords.

Pin Diagram of IC 7476 JK Flip Flop

 

Circuit Diagram D Flip flop :

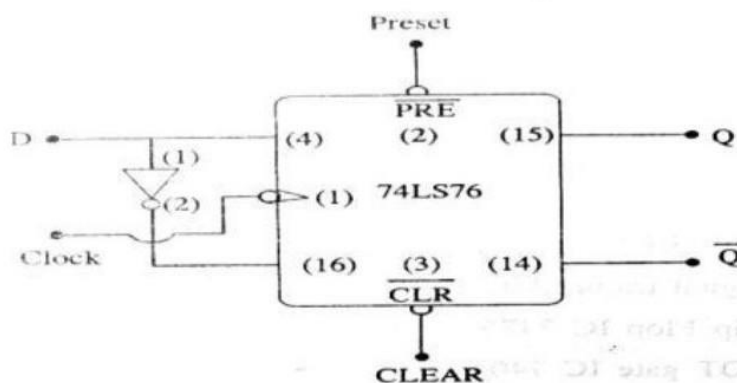


Note : Pin 5 = V_{cc} and 13 = GND for IC 7476.
 $\overline{\text{PRESET}} = V_{cc}$. $\overline{\text{CLEAR}} = V_{cc}$.

Truth Table of D Flip Flop

CLOCK	D	Q+	$\bar{Q} +$
0	X	Q	\bar{Q}
1	0	0	1
1	1	1	0

Circuit Diagram T Flip Flop :

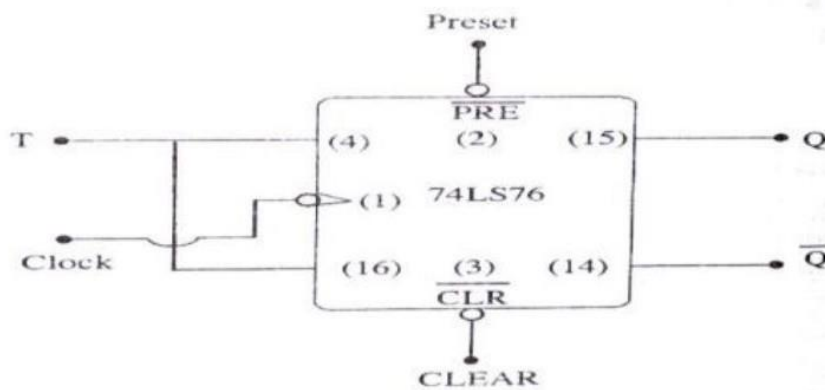

*Note : Pin 5 = V_{CC} and 13 = GND
PRESET = V_{CC}, CLEAR = V_{CC}.*

T	Q _{n+1}
0	Q _n
1	\bar{Q}_n

T	Previous		Next	
	Q _{Prev}	Q' _{Prev}	Q _{Next}	Q' _{Next}
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

Procedure :

1. Check the working of all the components.
2. Insert the appropriate IC into the IC base.
3. Make connections as shown in the circuit diagram.
4. First connect CLR pin to GND and apply one clock pulse so that initially 0 is loaded
5. Then change CLR to VCC and apply clock pulses and input
6. Verify the Truth Table and observe the outputs.

Result :


D-FF and T-FF are realized using JK FF IC 7476 and verified.

Week-8

Experiment – 1

Aim : Verilog description of SR flip flops using data flow modeling.

Logic Diagram

 

Truth table


S	R	Q	Q ₊₁	STATE
0	0	0	X	INVALID
0	0	1	X	INVALID
0	1	0	1	SET
0	1	1	1	SET
1	0	0	0	RESET
1	0	1	0	RESET
1	1	0	0	NC
1	1	1	1	NC

Verilog Code

```
module srfp (s, r, q, q_n);  
input s, r;  
output q, q_n;  
assign q_n = ~(s | q);  
assign q = ~(r | q_n);  
endmodule
```

Verilog description of JK flip flop using behavioral modeling

Logic Diagram

 

Truth Table

CP	J	K	Q_{n+1}	State
1	0	0	Q_n	NO CHANGE
1	0	1	0	RESET
1	1	0	1	SET
1	1	1	\bar{Q}_n	TOGGLES

Verilog Code:

```
module jkflip_df (j,k,q,qn);
input j,k,q;
output qn;
wire w1,w2;
assign w1=~q;
assign w2=~k;
assign qn=(j & w1 | w2 & q);
endmodule
```


Result: output for SR & JK Flip Flop is verified successfully

Week-8

Experiment – 2

Aim: Verilog description of T flip flops using behavioral modeling

Block Diagram

 

Truth Table

CLK	T	Q	Qb	OPERATION
0	x	Q	Qb	No Change
1	0	Q	Qb	No Change
1	1	Qb	Q	Toggle

Verilog Code

```
module t_ff(t, clk, rst, q,
qb);input t, clk, rst;
output q,
qb;reg q,qb;
reg
[22:0]div;
reg clkdiv;
always @ (posedge
clk) begin
div =
div+1'b1;
clkdiv =
div[22]; end
always @ (posedge
clkdiv) begin
if
(rst==1
)begin
q=0;
qb=1
;end
else
case
(t)
1'b0 : begin q=q; qb=qb; end
1'b1 : begin q=~(q); qb=~(qb);
enddefault: begin end
endcase
end
endmodule
```

Aim: Verilog description of D flip flops using behavioral modeling

Block Diagram



Truth Table

CLK	D	Q	Qb
0	X	X	X
1	0	0	1
1	1	1	0

Verilog Code

```
module d_ff(d, rst, clk, q,  
qb);input d;  
input rst,  
clk; output q  
,qb; reg  
q,qb;  
always@(posedge  
clk) begin  
if  
(rst==1)  
begin  
q=0;  
qb=1;  
end  
else  
begin  
q=d;  
qb=~d  
;end  
end  
endmodule
```

Result: output for D & T Flip Flop is verified successfully


Week-9

Experiment – 1

Aim : To Construct and verify the working of the following using suitable IC in digital trainer kit -SISO, SIPO, PISO and PIPO (4-bit) shift registers.

SHIFT REGISTERS USING 7495

SISO:

 


Example:

Count time	Ds	Q0	Q1	Q2	Q3
to	1	*	*	*	*
t1	0	1	*	*	*
t2	1	0	1	*	*
t3	1	1	0	1	*
t4	*	1	1	0	1
T5	*	*	1	1	0
T6	*	*	*	1	1
T7	*	*	*	*	1

Procedure:

- Connect the circuit as shown in circuit diagram
- To load serial data, make $P_E = 0$, and connect Cp1 to mono clock pulse
- Apply the clock pulses (t0 – t3) and load the serial data to the serial data i/p Ds
- Apply clock pulses (t4 – t7) and obtain the serial data o/p at Q3

SIPO(Right shift):

 


Example:

Count time	Ds	Q0	Q1	Q2	Q3
to	1	*	*	*	*
t1	0	1	*	*	*
t2	1	0	1	*	*
t3	1	1	0	1	*
t4	*	1	1	0	1


procedure:

- > Connect the circuit as shown in circuit diagram
- > To load serial data, make $P_E = 0$, and connect Cp1 to mono clock pulse
- > Apply the clock pulses (t0 - t3) and load the serial data to the serial data i/p Ds
- > Apply clock pulses (t4) and obtain the parallel o/p at Q3, Q2, Q1, Q0

PISO:

 

PIPO:

 

Example:

Clock	Time	Q ₀	Q ₁	Q ₂	Q ₃
Cp2	t ₀	*	*	*	*
	t ₁	1	0	1	1
Cp1	t ₂	*	1	0	1
	t ₃	*	*	1	10
	t ₄	*	*	*	1
	t ₅	*	*	*	*

→ PIPO
→ PISO

Procedure: a) PIPO :

- Connect the circuit as shown in circuit diagram
- To load parallel data, make $P_E = 1$, and connect Cp2 to mono clock pulse
- Load the data at P_3, P_2, P_1, P_0
- Apply Cp2 once and obtain the parallel o/p at Q_3, Q_2, Q_1, Q_0

Procedure: a) PISO :


- Connect the circuit as shown in circuit diagram
- To load parallel data, make $P_E = 1$, and connect Cp2 to mono clock pulse
- Load the data at P_3, P_2, P_1, P_0
- To shift data, make $P_E = 0$ and connect Cp1 to mono clock pulse.
- Apply clock pulse (t2 – t5) and obtain the serial data o/p at Q_3 .

Result : 4-bit SISO, SIPO. PISO and PIPO are realized using shift register IC 7495 and tabulated the data movement in each mode

Week-9 Experiment – 2


Aim: Construct and verify the working of the following using suitable IC in digital trainer kit - Ring and Johnson counter (4-bit).

RING COUNTER USING 7495:

 

Mode	Clock	QA	QB	QC	QD
1	1	1	0	0	0
0	2	0	1	0	0
0	3	0	0	1	0
0	4	0	0	0	1
0	5	1	0	0	0
0	6	repeats			

JOHNSON COUNTER USING 7495

 

Mode	Clock	QA	QB	QC	QD
1	1	1	0	0	0
0	2	1	1	0	0
0	3	1	1	1	0
0	4	1	1	1	1
0	5	0	1	1	1
0	6	0	0	1	1
0	7	0	0	0	1
0	8	0	0	0	0
0	9	1	0	0	0
0	10	repeats			

Procedure:

1. Check the working of all components
2. Insert the appropriate IC into IC Base
3. Make connections as shown in the circuit diagrams.
4. Apply the inputs, verify the Truth Table of the respective circuit and observe the outputs.

Result : Ring counter and Johnson counter using shift registers is implemented & output is verified

Week-10 Experiment – 1

3 bit ripple counter using IC 7476 :

Aim :

To Realize and verify the operation of 3-bit ripple counter using IC 7476.

Apparatus Required :

- ☞ Digital trainer kit
- ☞ JK Flip Flop IC 7476
- ☞ Patch chords.

Pin Diagram of IC 7476 JK Flip Flop


 


Diagram of 3-bit Ripple Counter

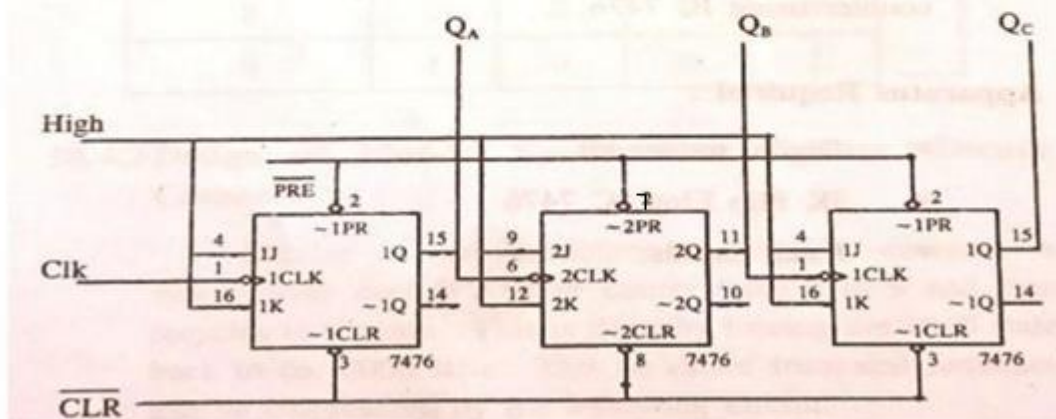

Truth Table of 3-bit Ripple Counter

Clock Pulse	Q _A	Q _B	Q _C
0	0	0	0
1	1	0	0
2	0	1	0
3	1	1	0
4	0	0	1
5	1	0	1
6	0	1	1
7	1	1	1
8	0	0	0

Procedure :

1. Check the working of all the components.
2. Insert the appropriate IC into the IC base.
3. Make connections as shown in the circuit diagram.
4. Apply GND to CLR (CLEAR pin 3 & 8) and apply one clock pulse to reset the counter to 000.
5. connect V_{CC} to CLR and PRESET (CLEAR pin 3 & 8, PRESET pins 2 & 7).
6. Apply the clock pulse manually.
7. Verify the Truth Table of the counter and observe the outputs.


Result :

The operation of 3-bit ripple counter using IC 7476 is verified.

Week-11 Experiment – 1

Aim: Verilog description for BCD up/down counter using behavior modeling

Block Diagram

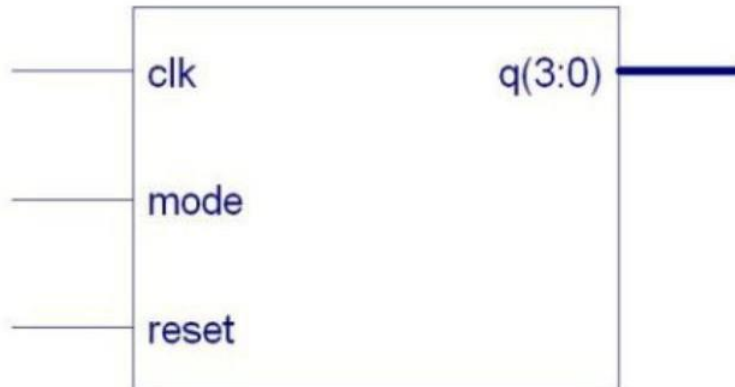

Truth Table

Clock Count	Output bit Pattern				Decimal Value
	QD	QC	QB	QA	
1	0	0	0	0	0
2	0	0	0	1	1
3	0	0	1	0	2
4	0	0	1	1	3
5	0	1	0	0	4
6	0	1	0	1	5
7	0	1	1	0	6
8	0	1	1	1	7
9	1	0	0	0	8
10	1	0	0	1	9

Verilog Code:

```

module updown
(clk,reset,mode,q); input
clk,reset,mode;
output[3:0]q;
reg[3:0]q;
reg
[22:0]div;
reg clkdiv;
always @ (posedge
  clk) begin
div =
div+1'b1;

```



```
clkdiv =  
div[22]; end  
always @ (posedge  
clkdiv) begin  
if (reset)  
q=4'b0000  
;  
else  
if(mode)  
q=q+1'b1;  
else  
q=q-1'b1;  
end  
endmodule
```


Result : Output for BCD up/down counter using behavior modeling is verified.

Week - 11

Experiment - 2

Aim:- Construct / Simulate and verify the working of R-2R DAC

 Apparatus:- IC 741, 1KΩ, 2.2KΩ Resistor, Connecting wires & multimeter



Tabular Column

Digital Inputs				Analogue output
D ₃	D ₂	D ₁	D ₀	
0	0	0	0	0
0	0	0	1	0.2083
0	0	1	0	0.4166
0	0	1	1	0.6249

Procedure:-

- 1) Check the working of all components
- 2) Make connections as shown in the circuit diagram
- 3) Apply various combinations of the input & verify the output
- 4) Calculate the theoretical value and verify practical value.

Result:- The working of R-2R DAC is verified successfully

Analogue output voltage for a 4-bit DAC is given as
Example 1000

$$V_0 = [2^3 D_3 + 2^2 D_2 + 2^1 D_1 + 2^0 D_0] \left[\frac{V_{ref}}{2^n} \right] \times \left[\frac{2R}{3R} \right]$$

$$= [2^3 \cdot 1 + 0 + 0 + 0] \left[\frac{5}{16} \right] \left[\frac{2}{3} \right]$$

$$V_0 = 8 \times \frac{5}{16} \times \frac{2}{3} = \frac{5}{3} \text{ V (Theoretical)}$$

$$V_0 = \frac{V_{ref} \cdot R}{R + 2R} = \frac{5 \times R}{3R} = \frac{5}{3} \text{ V (practical)}$$

1.6V

D₀ being LSB & D₃ being MSB bit

